

# **Concept Creation and Design of a Parameterizable, fast-locking 65 nm CMOS CDR-PLL for Gigabit Serial Chip-to-Chip Communication in Mobile Devices**

*by*

**Milan Forcan**

**Prof. Dr.-Ing. Klaus Solbach**  
University of Duisburg-Essen  
Department of Microwave and RF-Technology

**Reimund Wittmann    Markus Müller    Ralf Kakerow**  
Nokia Research Center Bochum


**Prof. Dr.-Ing. Werner Schardein**  
University of Applied Sciences Dortmund

# Contents

- Introduction
- Clock and Data Recovery Architectures
  - Clock and Data Recovery PLL
  - Oversampling CDR
- Analysis of Clock and Data Recovery Circuits
  - Simulation Environment
  - Hogge PD vs. Alexander PD
- CDR-PLL Implementation
  - Generic Engineering Model
  - CDR-PLL Building Blocks

# Introduction

- Basic structure of a serial data link:

 


- Serial data transmission with embedded clock
- How to determine which bit is sent?
- Solution: **Clock and Data Recovery Circuit**
  - Extract the clock signal and align it to data
  - Resample the noisy analog data signal
- Challenges:
  - **Extremely fast locking time compared to conservative CDR**
  - **Sufficient jitter performance**

# Contents

- Introduction
- Clock and Data Recovery Architectures
  - Clock and Data Recovery PLL
  - Oversampling CDR
- Analysis of Clock and Data Recovery Circuits
  - Simulation Environment
  - Hogge PD vs. Alexander PD
- CDR-PLL Implementation
  - Generic Engineering Model
  - CDR-PLL Building Blocks
 
# Clock and Data Recovery PLL I

First approach: **Phase-Locked Loop (PLL)**






- **Phase Detector:** Generates an output signal in relation to the phase difference of both inputs
- **Charge-Pump:** Output pulses of PD are converted to current
- **Low-Pass Filter:** Integrates the output of the charge pump and produces the control voltage
- **Voltage Controlled Oscillator:** Generates a periodic output whose frequency depends on the control voltage

# Clock and Data Recovery PLL II
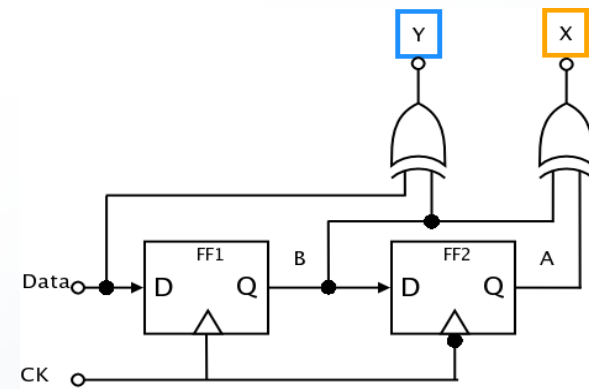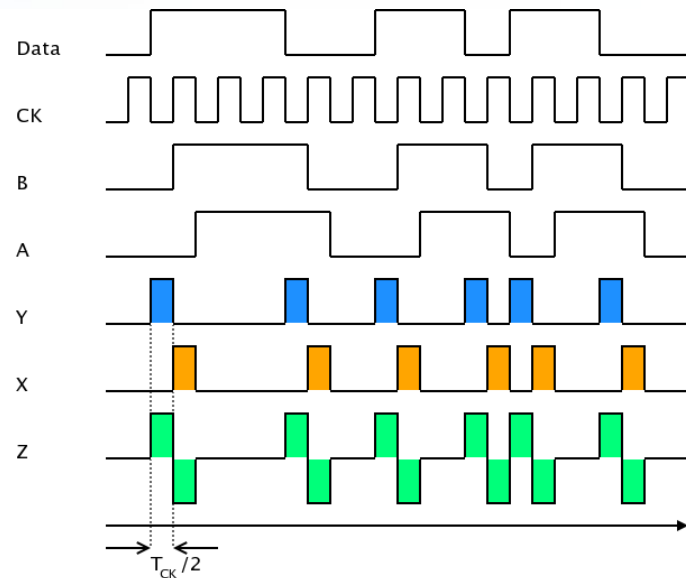 
## Hogge Phase Detector (Linear PD):



- Path Y produces *proportional pulses* in relation to phase difference
- Path X produces  $T_{ck}/2$  wide *reference pulses*
- Under locked condition Y & X show pulses with equal width



# Clock and Data Recovery PLL III
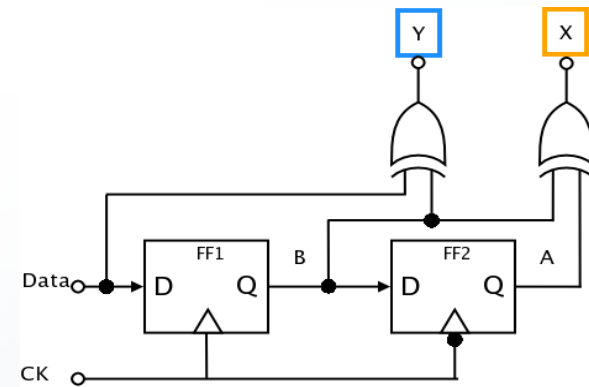 
## Hogge Phase Detector (Linear PD):

- **Benefits:**
  - Linear dependence between output and phase difference
  - Wide frequency acquisition range
  - Linear behaviour enables loop parameters calculation
- **Drawback:**
  - “Triwaves” are produced, resulting in noise on oscillator line
  - Clock skew due to internal delays



# Clock and Data Recovery PLL IV

## Alexander Phase Detector (Bang-Bang PD):



- Data is sampled at 3 equidistant points A, B and C
- XOR gates combine nodes A, B and C:

$$X = A \text{ xor } B \text{ and } Y = B \text{ xor } C$$

- Performs an **early-late detection**

Clock is **early**:  $Y = Low$  and  $X = High$

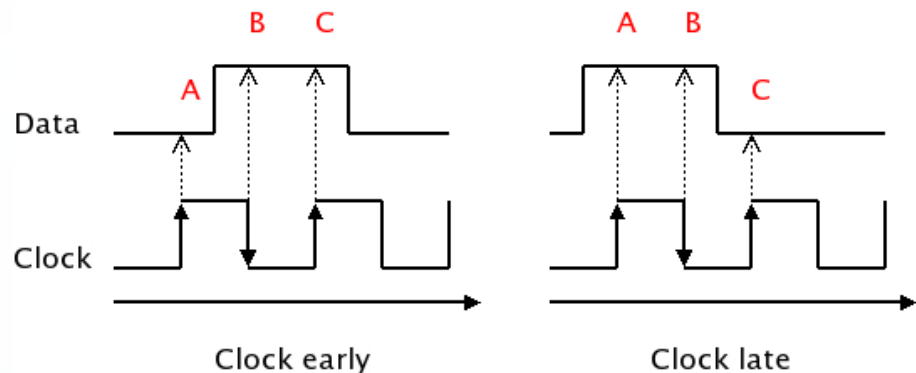
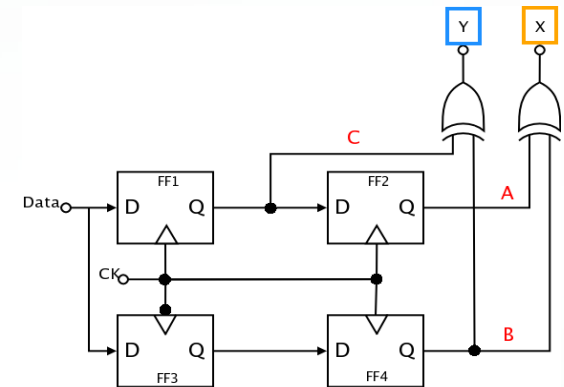
Clock is **late**:  $Y = High$  and  $X = Low$






# Clock and Data Recovery PLL V
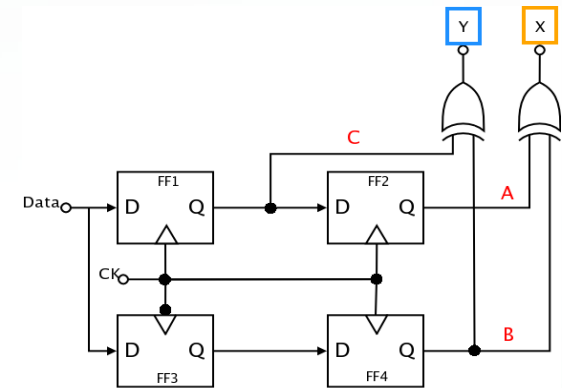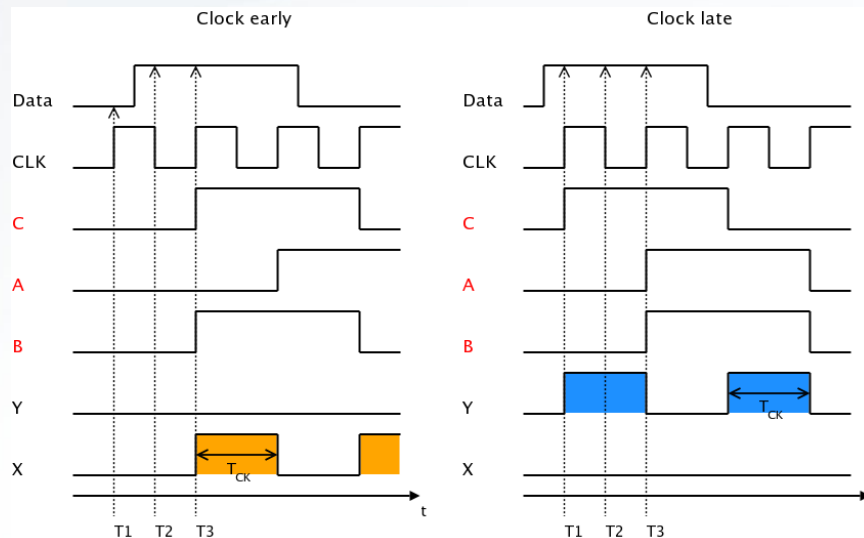
## Alexander Phase Detector (Bang-Bang PD):



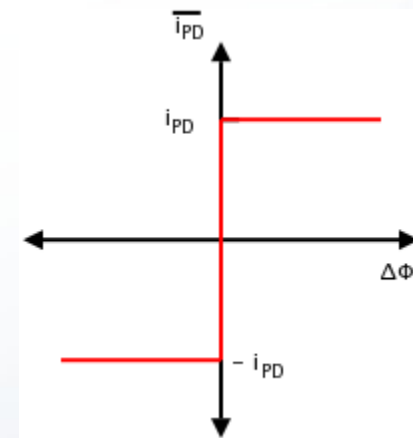- **Benefit:**
  - In steady state clock is aligned in the middle of the data eye
- **Drawback:**
  - Small frequency capture range



# Contents

- Introduction
- **Clock and Data Recovery Architectures**
  - Clock and Data Recovery PLL
  - **Oversampling CDR**
- Analysis of Clock and Data Recovery Circuits
  - Simulation Environment
  - Hogge PD vs. Alexander PD
- CDR-PLL Implementation
  - Generic Engineering Model
  - CDR-PLL Building Blocks

# Oversampling CDR

Second approach: **Oversampling CDR**


1. Sample data at equidistant points
2. Detect data transition occurrence
3. Select clock phase to resample the data

- **Benefits:**

- Digital implementation
- Very fast acquisition

- **Drawbacks:**

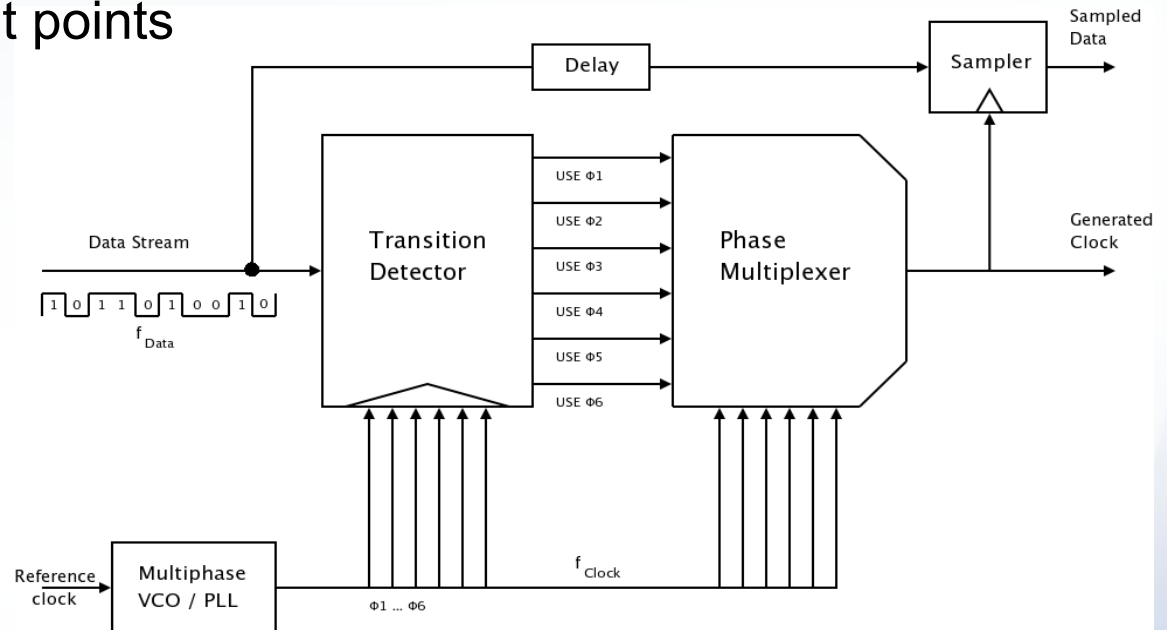- Design complexity increases with frequency and jitter requirements
- Additional multiphase VCO/PLL needed





# Contents

- Introduction
- Clock and Data Recovery Architectures
  - Clock and Data Recovery PLL
  - Oversampling CDR
- Analysis of Clock and Data Recovery Circuits
  - Simulation Environment
  - Hogge PD vs. Alexander PD
- CDR-PLL Implementation
  - Generator Driven Generic Engineering Model
  - CDR-PLL Building Blocks

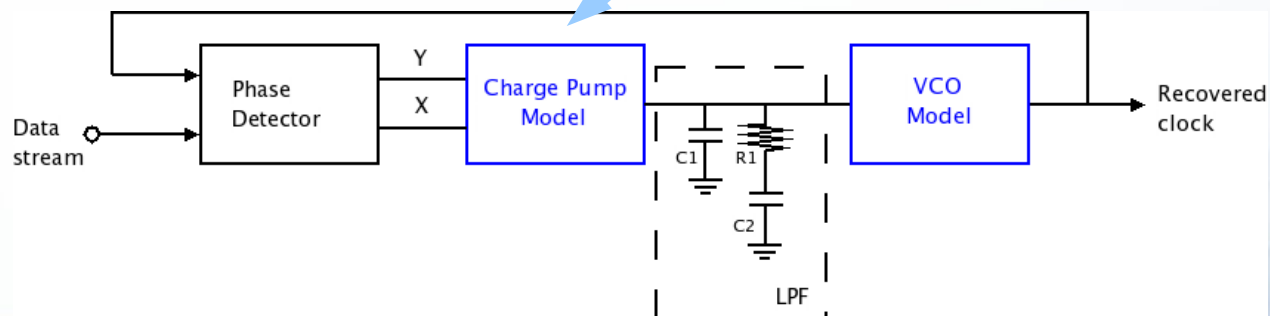
 
# Simulation Environment

- Implementation of appropriate models for first comparison of Hogge PD and Alexander PD
- SKILL code generates data stream:
  - 1.25 Gb/s ( $1UI = 800ps$ )
  - Pseudo-random
  - Adjustable Jitter
  - 8B10B-coding
- Verilog-A models:
  - Charge-Pump
  - Voltage Controlled Oscillator


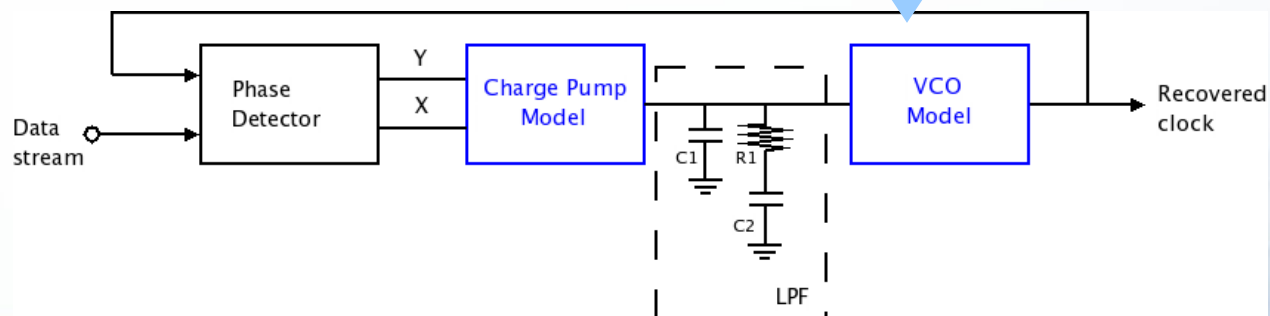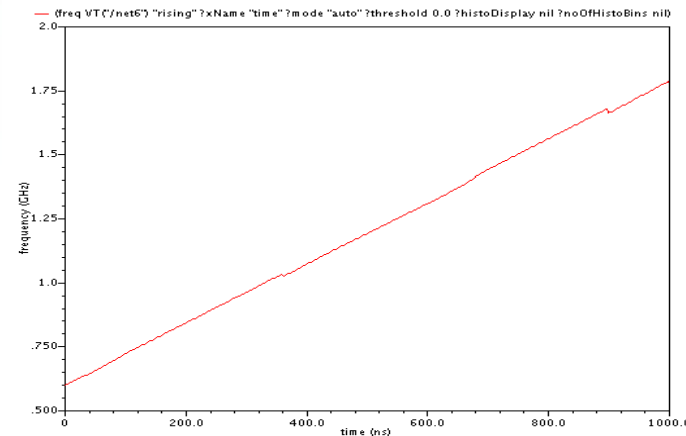
# Simulation Environment


- Implementation of appropriate models for first comparison of Hogge PD and Alexander PD
- SKILL code generates data stream:
  - 1.25 Gb/s ( $1UI = 800ps$ )
  - Pseudo-random
  - Adjustable Jitter
  - 8B10B-coding
- Verilog-A models:
  - Charge-Pump
  - Voltage Controlled Oscillator



# Hogge PD vs. Alexander PD I
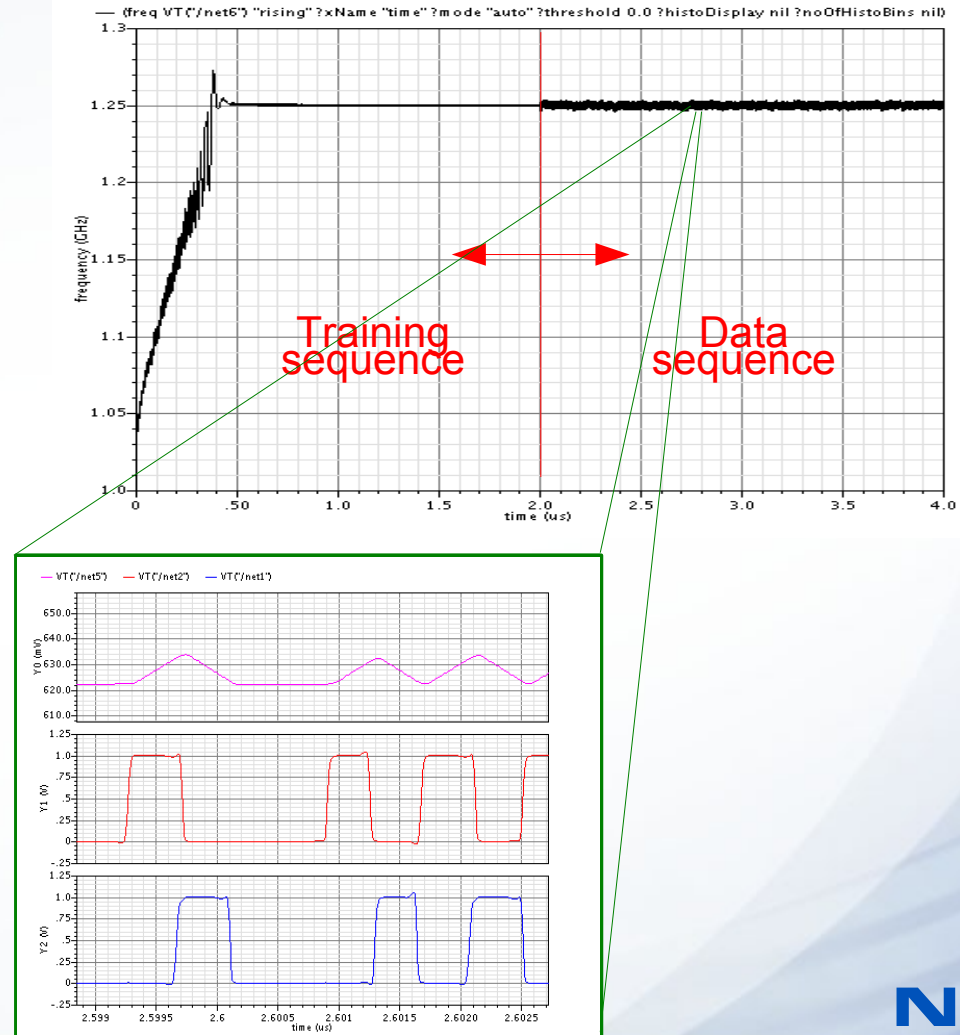
## Hogge PD simulation results:



- **Pro:**
  - Wide frequency acquisition range
  - Linear behaviour
  - Fast locking time of 500 ns (625 UI)
- **Contra:**
  - Triwaves on the oscillator line
  - Systematic clock skew of 150 ps (0.18 UI)



# Hogge PD vs. Alexander PD I
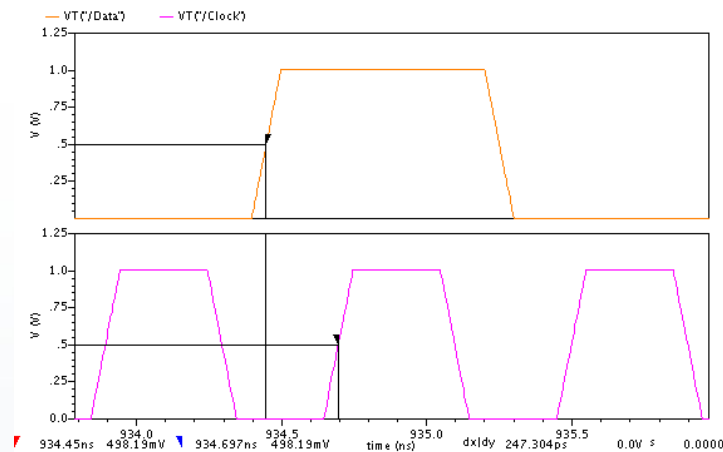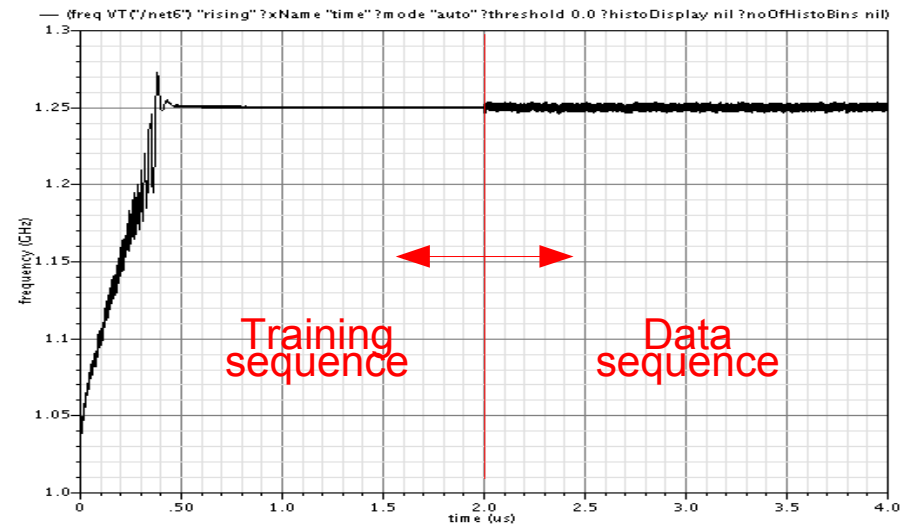
## Hogge PD simulation results:

- **Pro:**
  - Wide frequency acquisition range
  - Linear behaviour
  - Fast locking time of 500 ns (*625 UI*)
- **Contra:**
  - Triwaves on the oscillator line
  - Systematic clock skew of 150 ps (*0.18 UI*)






# Hogge PD vs. Alexander PD II
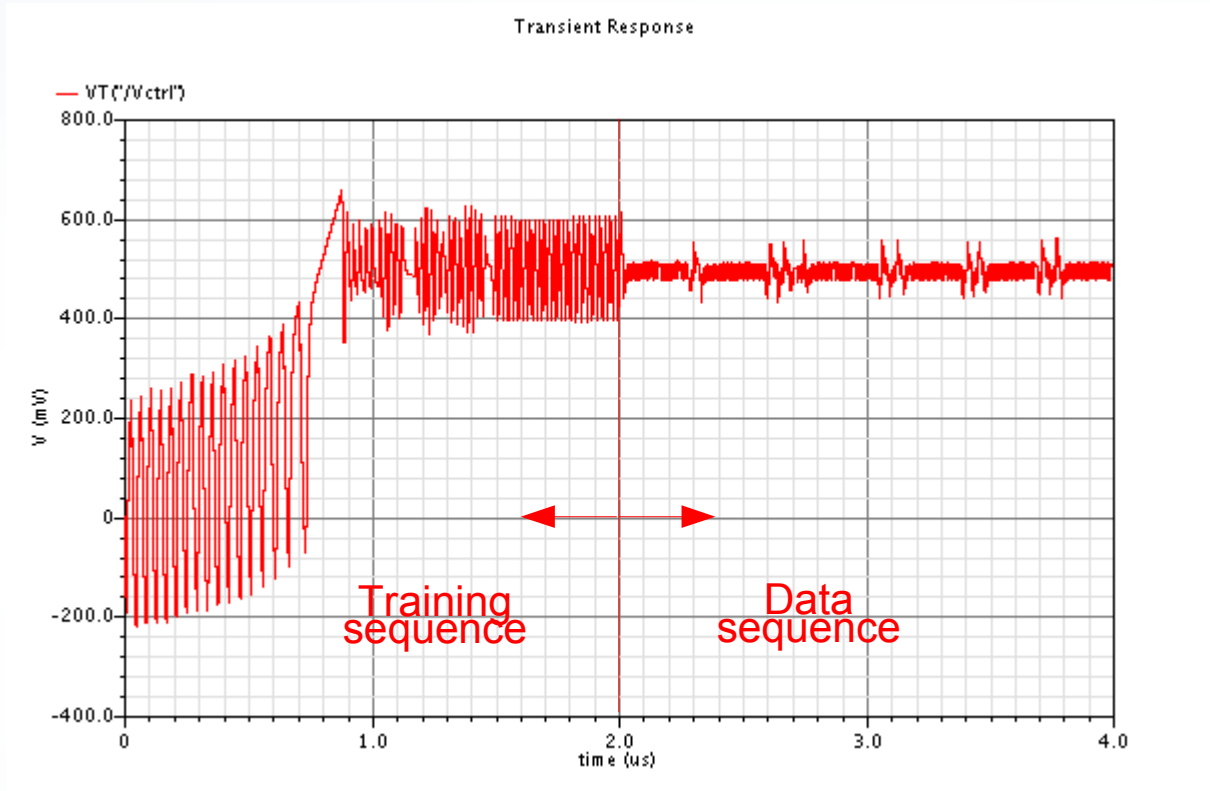
## Alexander PD simulation results:

- **Pro:**
  - Successful phase lock
- **Contra:**
  - Higher noise on oscillator line
  - Frequency acquisition range < 100 MHz!
  - Additional frequency detection required



# Circuit Selection

- Hogge PD:
  - Wide frequency acquisition range
  - Fast acquisition time
  - Acceptable output clock jitter
  - Triwaves and clock skew
- Alexander PD:
  - Successful lock
  - Narrow frequency acquisition range requires frequency detection
- Oversampling CDR approach:
  - Very fast acquisition time
  - High design efforts
  - More than 6 phases required for reasonable jitter performance

# Circuit Selection


- Hogge PD:
  - Wide frequency acquisition range
  - Fast acquisition time
  - Acceptable output clock jitter
  - Triwaves and clock skew
- ➔ Implementation of CDR-PLL using:
  - Hogge PD
  - Charge pump and LPF
  - Voltage Controlled Oscillator

# Contents

- Introduction
- Clock and Data Recovery Architectures
  - Clock and Data Recovery PLL
  - Oversampling CDR
- Analysis of Clock and Data Recovery Circuits
  - Simulation Environment
  - Hogge PD vs. Alexander PD
- CDR-PLL Implementation
  - Generic Engineering Model
  - CDR-PLL Building Blocks
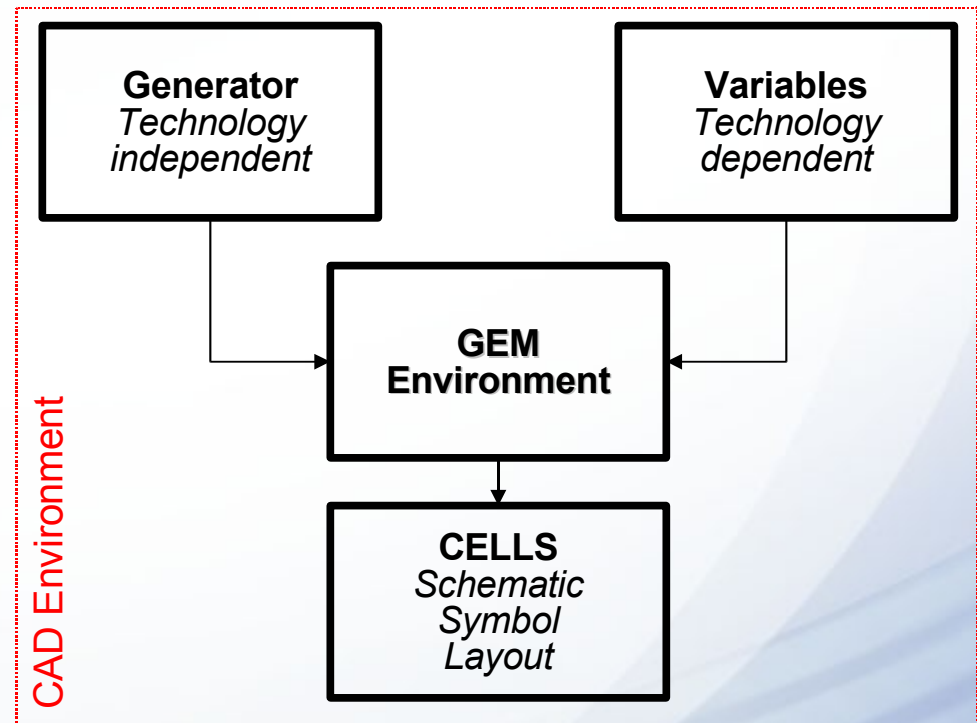
# Generic Engineering Model (GEM)

- C-like description generates schematic, layout and testbench
- Variables define technology dependent design rules
- Create instances, wires and contacts using functions
- **Benefits:**
  - Reusable circuit generators
  - Generator parameters allow fast modification of implemented circuit
  - Technology independent
  - Adaptable on common CAD systems (e.g. Mentor, Cadence)





# CDR-PLL Building Blocks I

## Modifications on Hogge PD:

- Correct clock skew using first delay
- Eliminate Triwaves using second delay
  
## Modifications on LPF:

- Capacitances  $C1 = 100 \text{ fF}$   
 $C2 = 1.9 \text{ pF}$
- Resistor  $R1 = 8.3 \text{ kOhms}$
- Loop transfer function:
  - Bandwidth  $f_{0dB} = 50.5 \text{ MHz}$
  - Phase margin  $PM = 65^\circ$
  - Overshoot = 1.29 dB





# CDR-PLL Building Blocks I

## Modifications on Hogge PD:

- Correct clock skew using first delay
- Eliminate Triwaves using second delay

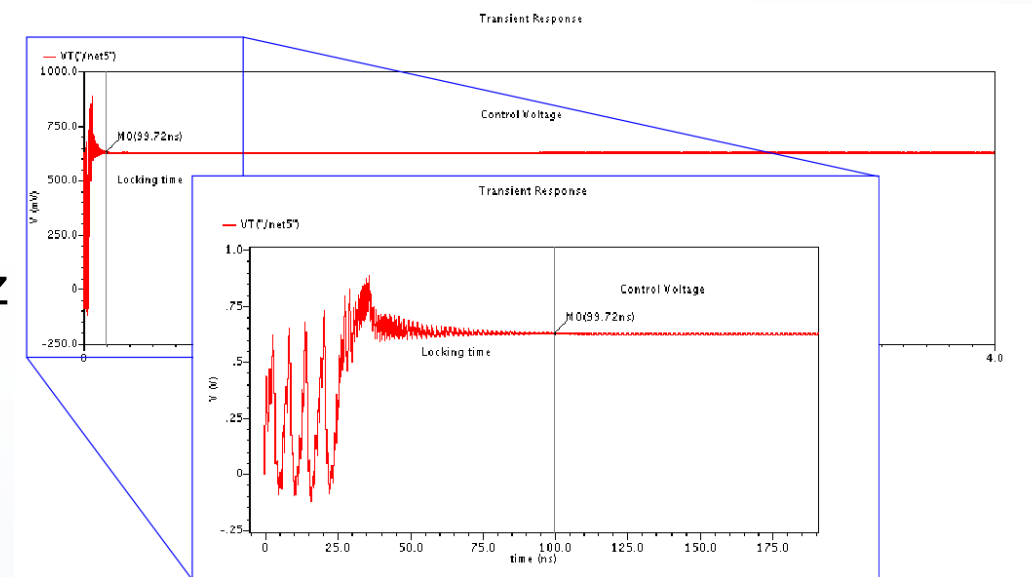 
## Modifications on LPF:

- Capacitances  $C1 = 100 \text{ fF}$   
 $C2 = 1.9 \text{ pF}$
- Resistor  $R1 = 8.3 \text{ kOhms}$
- Loop transfer function:
  - Bandwidth  $f_{0dB} = 50.5 \text{ MHz}$
  - Phase margin  $PM = 65^\circ$
  - Overshoot = 1.29 dB


 
# CDR-PLL Building Blocks II

- Current-Starved Voltage Controlled Oscillator:







# CDR-PLL Building Blocks III


- VCO specifications:
  - Operating point:  
1.25 GHz at 0.65V
  - Limited linear range
  - Tuning range:  
1.17 GHz – 1.42 GHz
  - VCO slope: 400 MHz/V
  - Parameter verification with layout simulation required

- VCO frequency characteristic:

 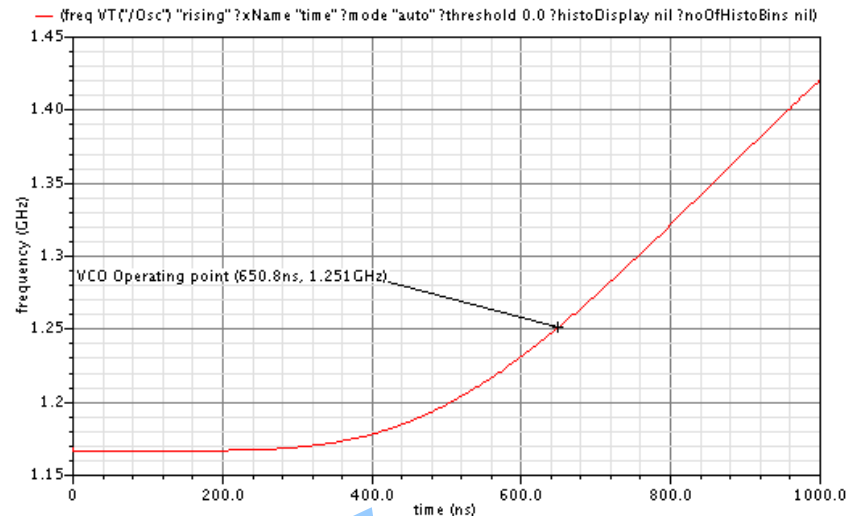


# CDR-PLL Building Blocks IV

- Current steering Charge Pump:

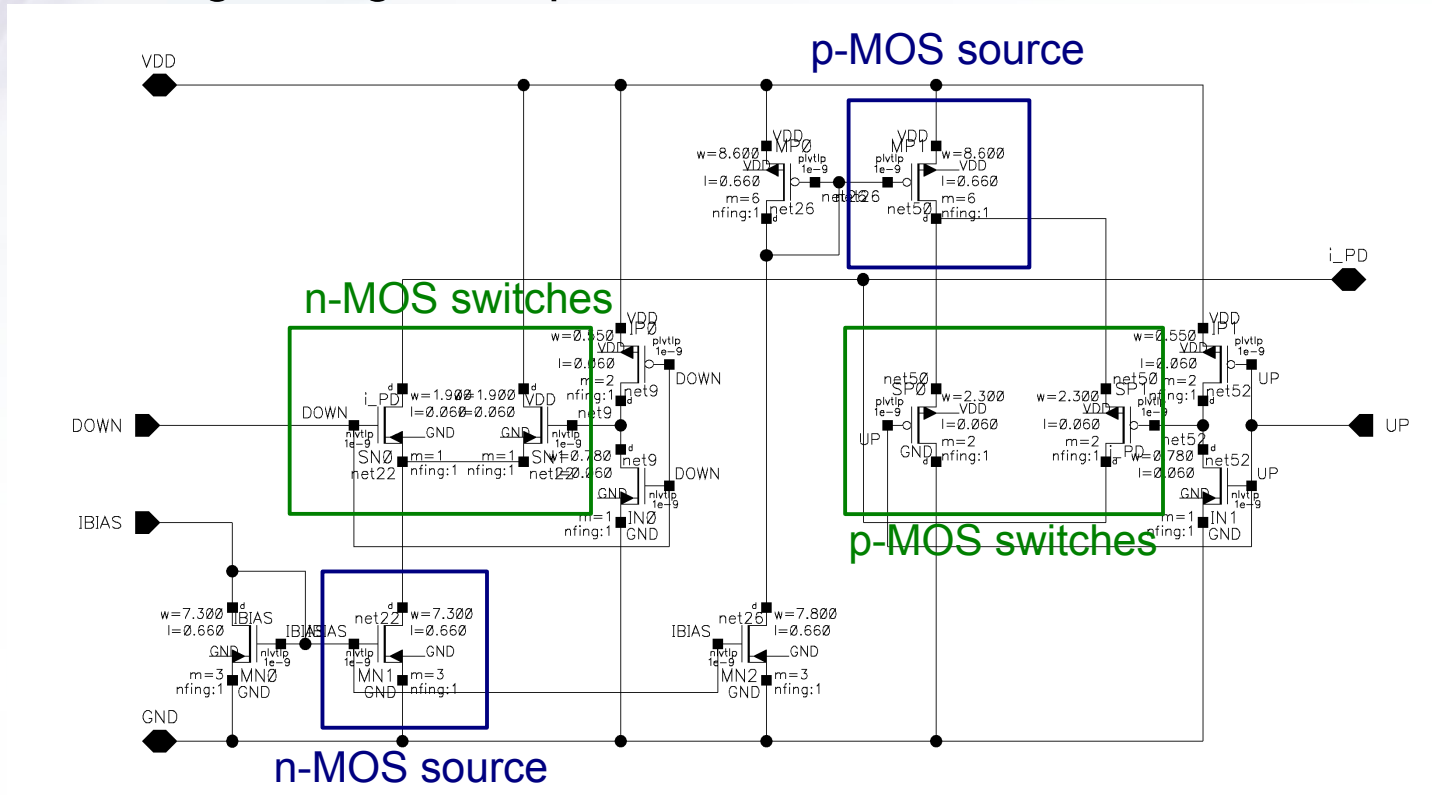


# CDR-PLL Building Blocks V

- Charge pump DC characteristic:

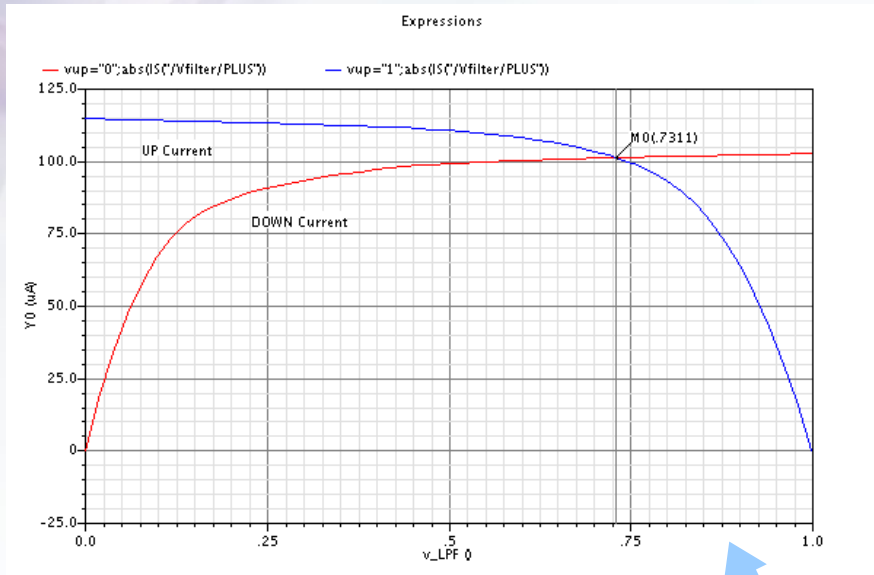



- Charge pump specifications:

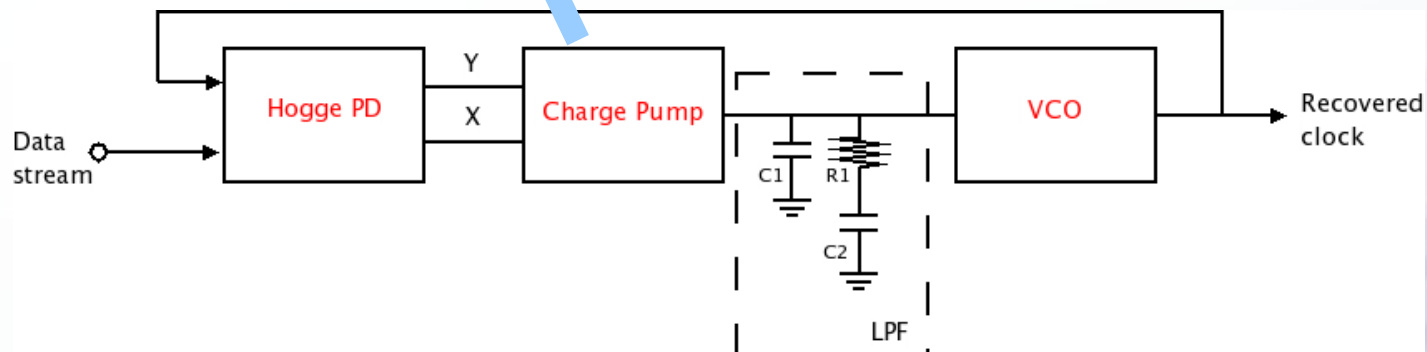- Suitable for high speeds
- Scalable currents
- Limited linear range
- 100  $\mu$ A at operating point


 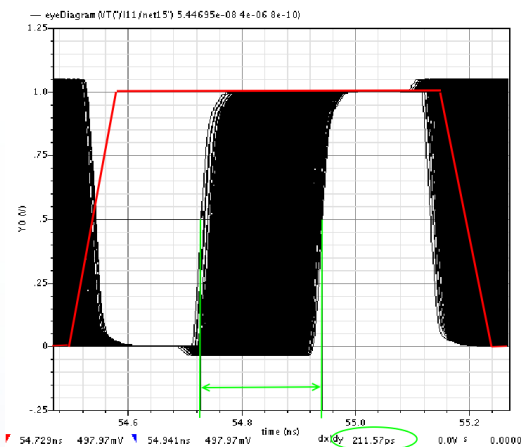
# Simulation Results


- Locking time: 55 ns  $\approx$  70 UI  
(up to 10x faster than conservative CDR-PLL)
- Input jitter tolerance: 0.39 UI at 1.25 GB/s verified  
(SATA compliant)
- Clock output jitter: 0.26 UI at 0.39 UI data jitter
- Power consumption: 0.615 mW at 1V
- CDR core dimensions: 100  $\mu$ m x 100  $\mu$ m



**Thank you for your attention!**


# Appendix

- VCO layout

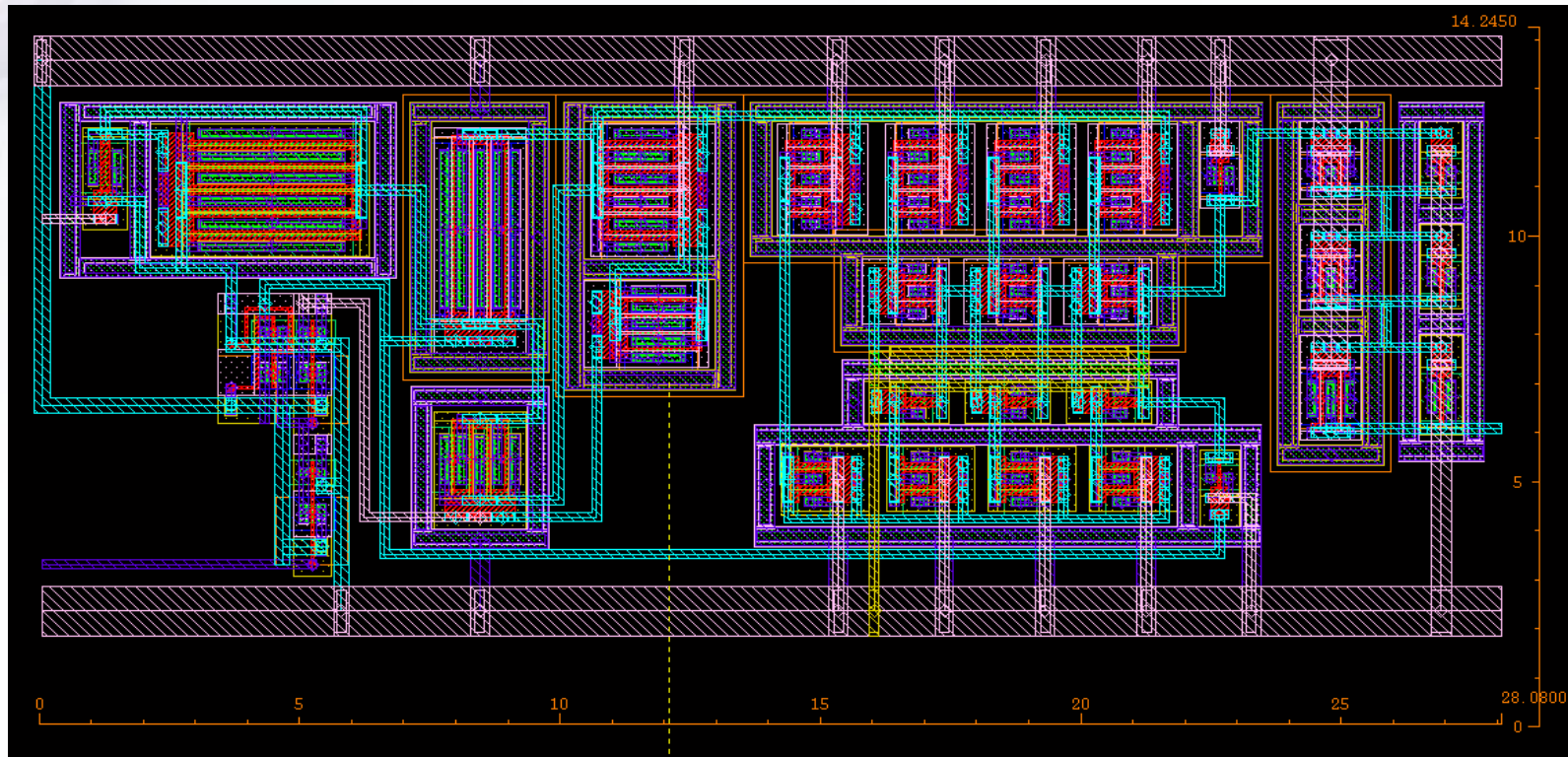


# Appendix

- Charge pump layout

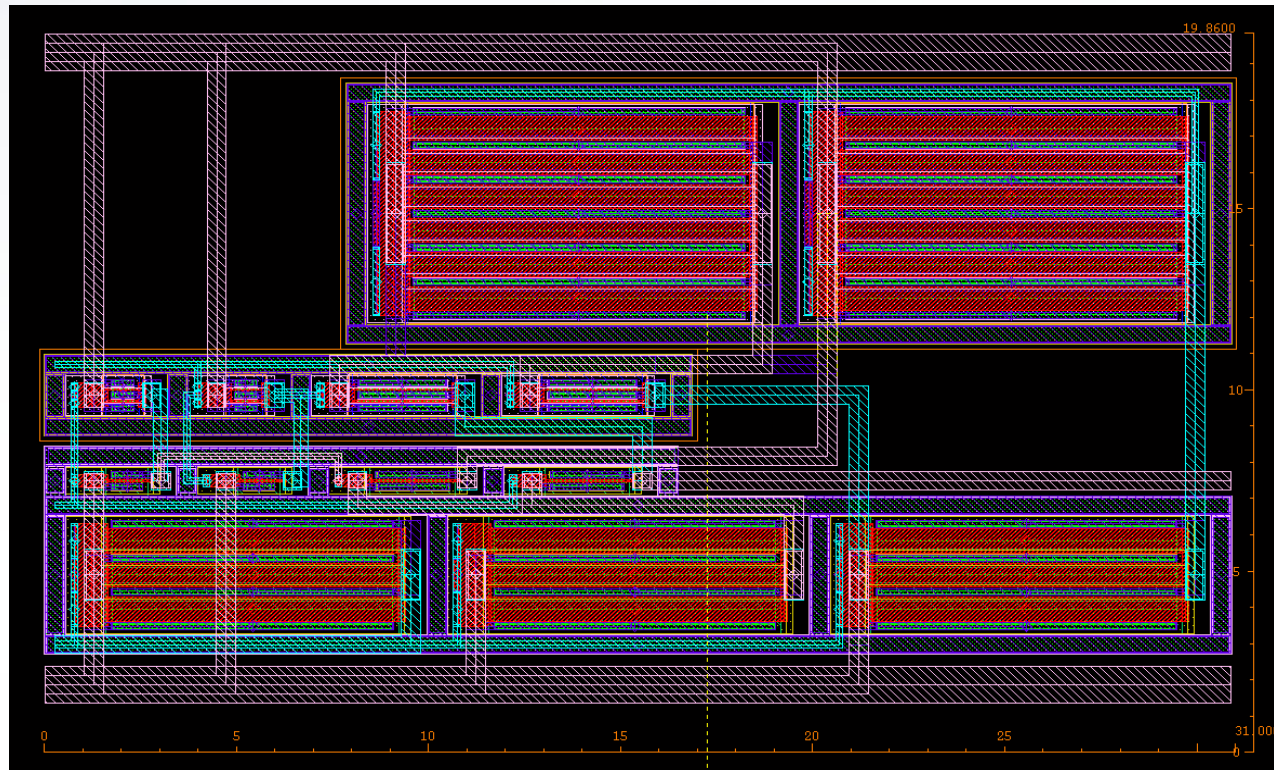


# Appendix

- Oversampling CDR (input stage):

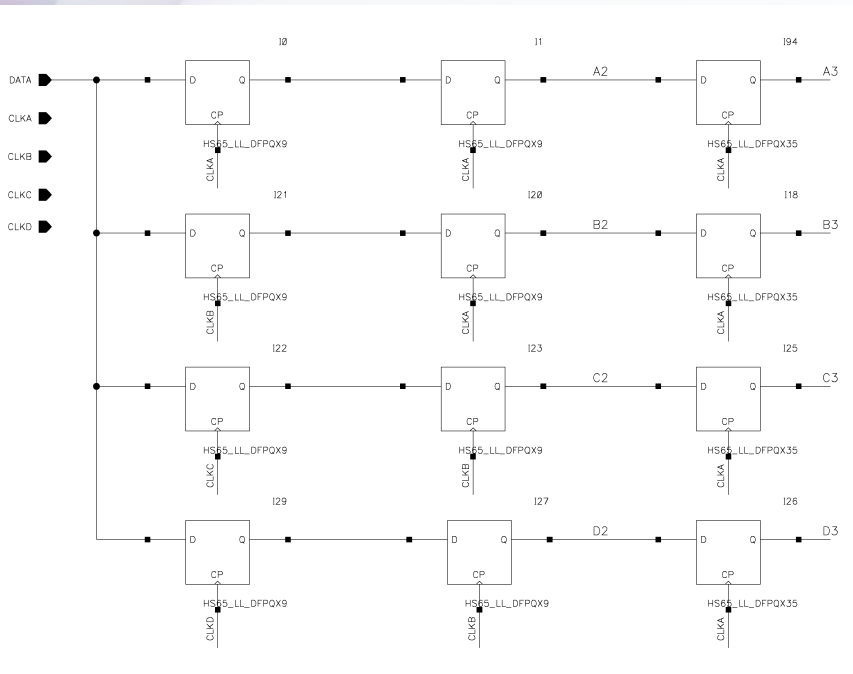

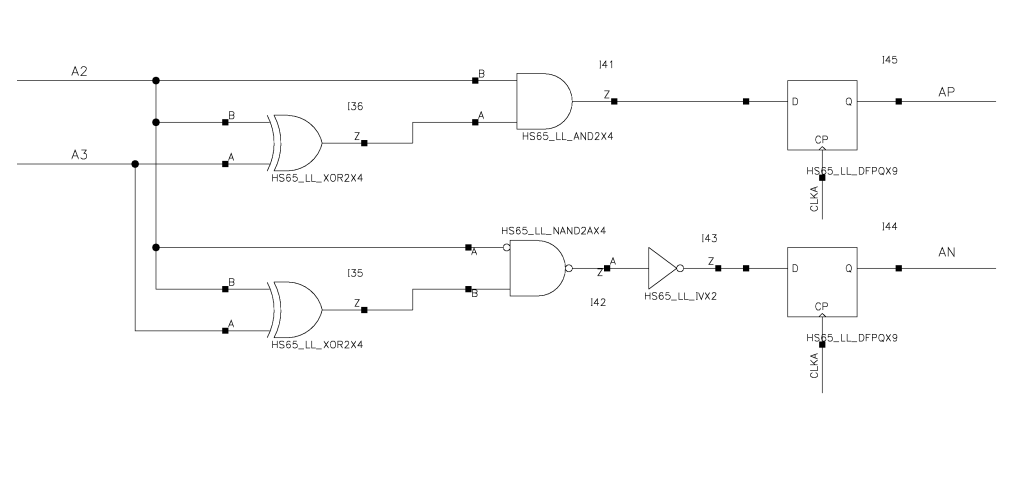
- Oversampling CDR (transition detection):





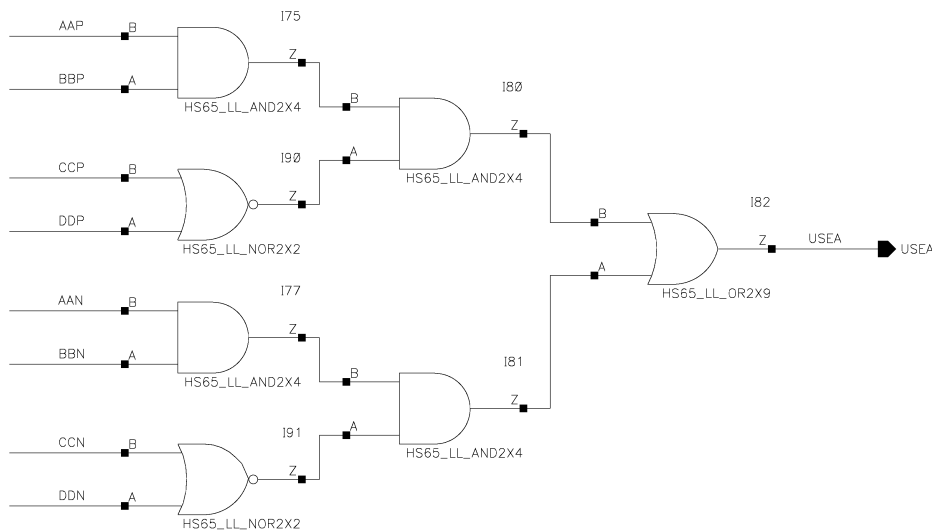
# Appendix

- Oversampling CDR (*USEA signal stage*):




 - Oversampling CDR (*USEC signal stage*):


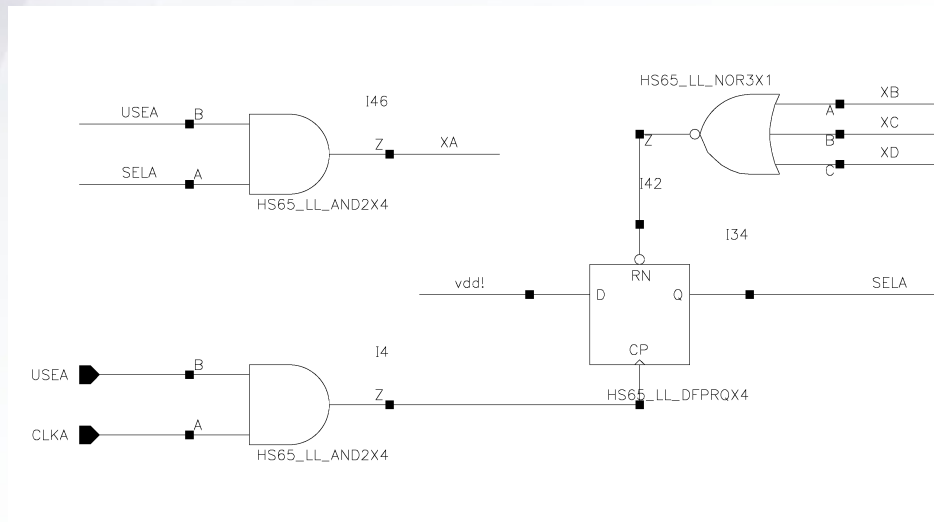
# Appendix

- Oversampling CDR (*SELA signal stage*):



- Oversampling CDR (*phase switching stage*):

